

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2018

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.**(SEM. I) EXAMINATION, 2007-08****ELECTRICAL ENGINEERING***Time : 3 Hours]**[Total Marks : 100*

1 Attempt any **four** parts of the following : 5×4=20

(a) Give analogous characteristics of electrical and magnetic ckts. 5

(b) An iron ring is made up of three parts : 5

$$l_1 = 10 \text{ cm}, \quad A_1 = 5 \text{ cm}^2, \quad l_2 = 8 \text{ cm},$$

$$A_2 = 3 \text{ cm}^2, \quad l_3 = 6 \text{ cm}, \quad A_3 = 2.5 \text{ cm}^2. \text{ It is}$$

wound with a coil of 250 turns. Calculate current required to produce flux of 0.4 mWb.

$$\mu_1 = 2670, \quad \mu_2 = 1050, \quad \mu_3 = 600.$$



- (c) Define parallel resonance. Calculate at resonance the resultant current and quality factor in terms of the parameters of a ckt. 5

- (d) Find applied voltage and power loss in a ckt. 5 shown below in Fig. 1.

The value of C is $20 \mu F$, Current $I = 0.345 A$.

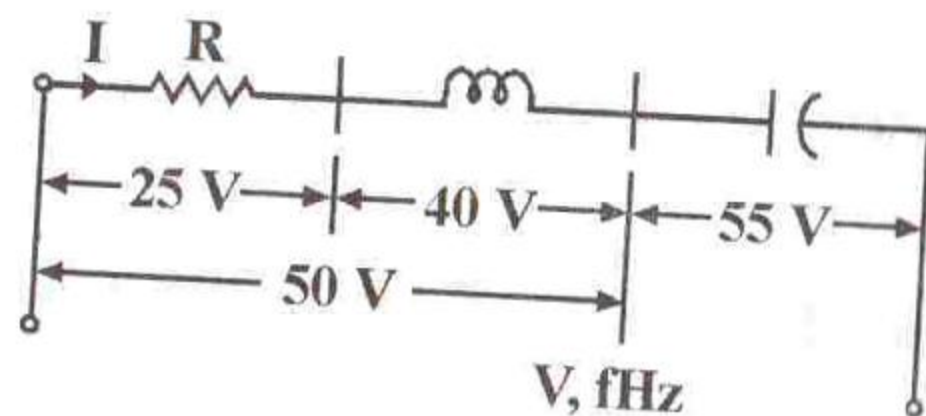


Fig. 1

- (e) $z_1 = (150 - j 157) \Omega$, $z_2 = (100 - j 110) \Omega$ 5

are connected in parallel at $200 V$, $50 Hz$ supply. Find :

- I_1 , I_2
- I_T (Total current)
- Total power
- P.F. and draw phasor diagram.

- (f) A series R-L-C ckt has 100Ω resistor, 0.318 HL, and C . $v = 230 \times \sqrt{2} \sin wt V$,

$$i = 2.3 \times \sqrt{2} \sin wt A$$

Find :

- C
- V_L
- Power

take $\omega = 314.15 \text{ rad/sec}$.

- 2 Attempt any **four** parts of the following : 5×4=20

- Obtain equivalent Y from Δ in Y- Δ transformation. 5
- Using Thevenin's theorem obtain current in 13Ω resistance in Fig. 2. 5

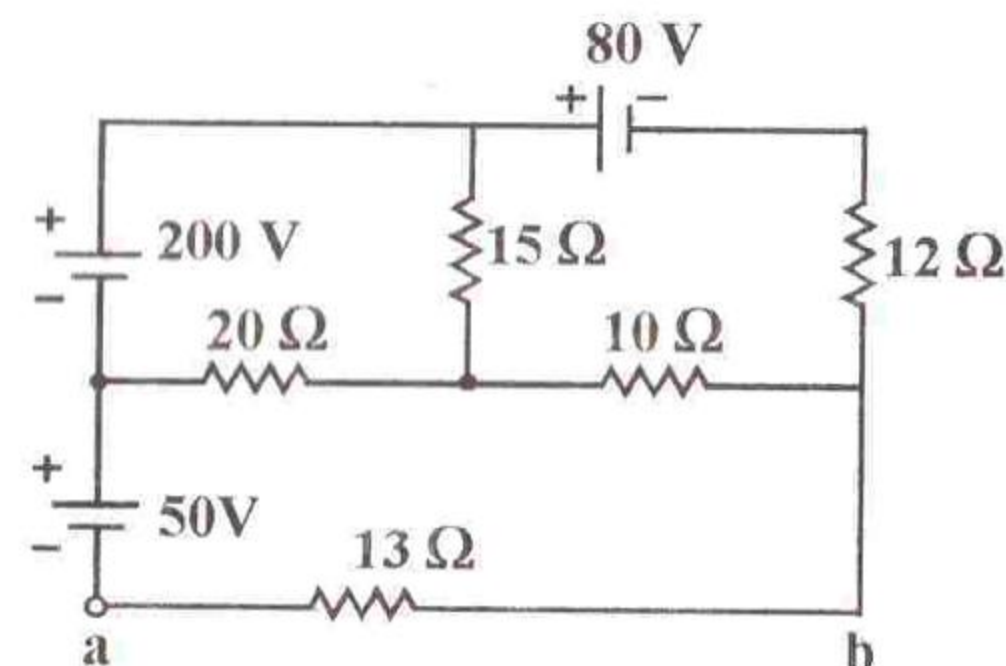


Fig. 2

- (c) Using Nodal analysis, find V_{cd} for the ckt. shown below in Fig. 3.

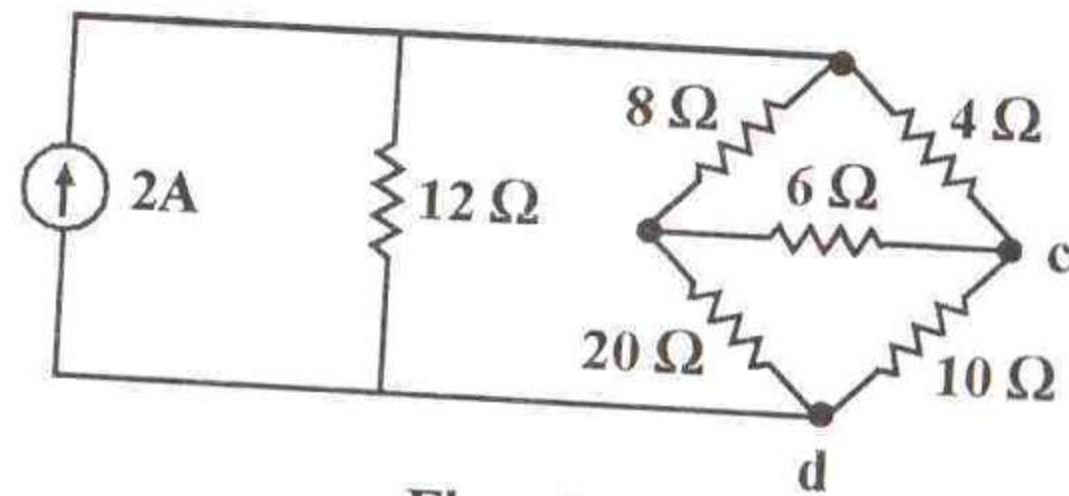


Fig. 3

- (d) State and prove superposition theorem taking an example. 5
- (e) Find the Norton's equivalent ckt. as seen by R_L in the following ckt : 5

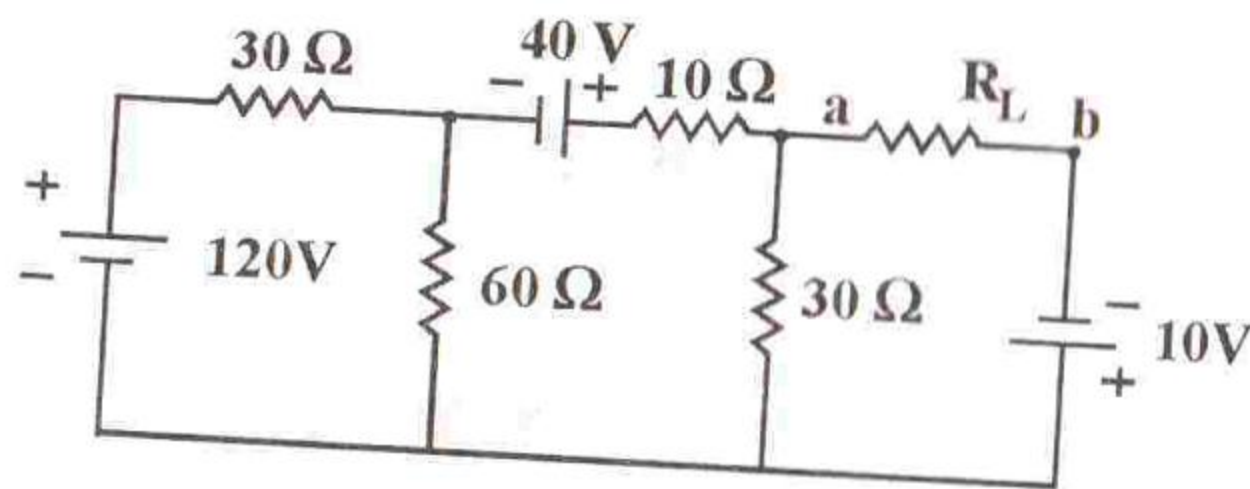


Fig. 4

- (f) Calculate average and rms value of a half sine wave. 5

3 Attempt any **two** parts of the following : 2×10=20

- (a) Explain two wattmeter method to measure 3- ϕ power in Y-connected load. Derive the phase angle in terms of wattmeter readings. Draw phasor diagram also. 10
- (b) A 3- ϕ , 3-wire, Y-connected system has 150 V between phase to phase. Each phase has $z = 5 \angle -30^\circ$. 10

Find :

- (1) Current in each phase
 - (2) Total power
 - (3) Draw phasor diagram.
- (c) Explain the OC and SC test performed on a single phase transformer. Determine the equivalent circuit based on the above test. Derive the condition for maximum efficiency of a transformer. 10

4 Attempt any **two** parts of the following : 2×10=20

- (a) What are different methods of speed control for DC motor ? Explain armature resistance control method. 10

(b) Explain principle of operation of synchronous motor. Give its applications. 10

(c) (i) Derive the emf equation for a dc machine. 10

(ii) A 4-pole dc generator with wave connected armature has 41 slots, and 12 conductors /slot.

Armature resistance $R_a = 0.5\Omega$. Shunt resistance is $R_{sh} = 200\Omega$. Flux per pole is

125 mWb. Speed $N = 1000$ rpm. Calculate voltage across 10Ω load resistance across the armature terminal.

5 Attempt any two parts of the following : $2 \times 10 = 20$

(a) Why single phase induction motor is not self starting? What are different methods to make it self starting? Explain one of them. 10

(b) Why starter is needed for 3- ϕ induction motor? Explain $Y - \Delta$ starter with neat and clean sketch. 10

(c) A 4-pole, 3- ϕ induction motor runs at 1440 rpm. Supply voltage is 500 V at 50 Hz.

Mechanical power output is 20.3 hp and mechanical loss is 2.23 hp. Calculate :

(i) Mechanical power developed

(ii) Rotor Cu loss

(iii) Efficiency.